

CHAPTER SEVENTEEN

MOS Digital Integrated Circuits

Digital Electronics.

Introduction

There are several MOS logic families used in digital ICs: NMOS, PMOS, CMOS (Complementary) , HCMOS (High density and High speed).

MOSFET transistors can be used as active devices and as load elements also.

We will emphasize on N-MOSFET (enhancement) in this chapter

General N-MOS Inverter

A generalized NMOS is shown below. The load device, may be a resistor or another MOSFET.

$$V_{IN} = V_{GS} + I_G R_G \quad \text{where } I_G = 0 \quad V_{IN} = V_{GS}$$

$$V_{OUT} = V_{DS}$$



Since I_G is negligible $I_{DD} = I_L = I_D$

In linear mode: $(V_{GS} \geq V_{TN}), V_{DS} \leq V_{GS} - V_{TN}$

$$I_{DS} = \frac{K_n}{2} [2 \times (V_{GS} - V_{TN}) V_{DS} - V_{DS}^2]$$

In active mode: $(V_{GS} \geq V_{TN})$
 $V_{DS} = 0$ Zero drain current

HOW??

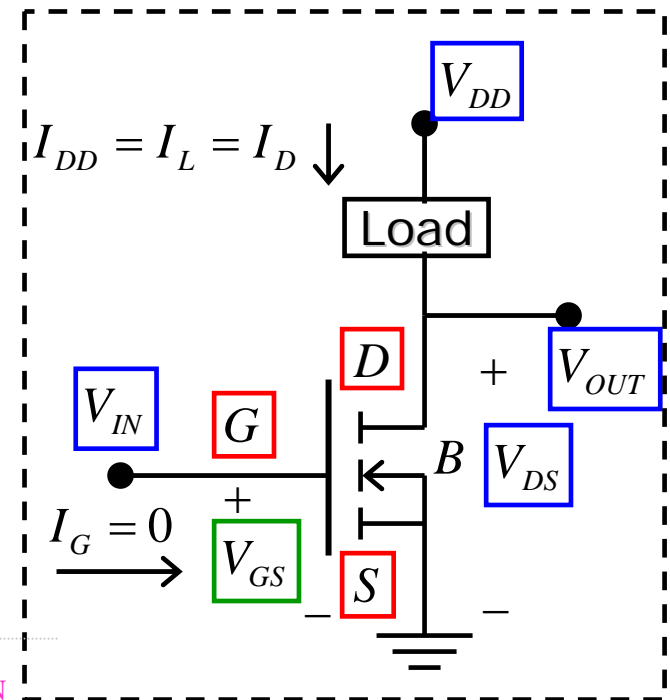 

Operation of N-MOS with Zero Drain Current

Graphical analysis:

If the drain current is forced to $I_D \sim 0$, then the drain-to-source voltage is also forced to $V_{DS} \sim 0$

Analytical analysis:

Setting $I_D \sim 0$ in the linear region gives:

$$0 = \frac{K_n}{2} [2 \times (V_{GS} - V_{TN}) V_{DS} - V_{DS}^2]$$




$$V_{DS} [2(V_{GS} - V_{TN}) - V_{DS}] = 0$$

$$V_{DS} = 0 \quad \checkmark$$

$$V_{DS} = 2(V_{GS} - V_{TN}) \quad \times$$

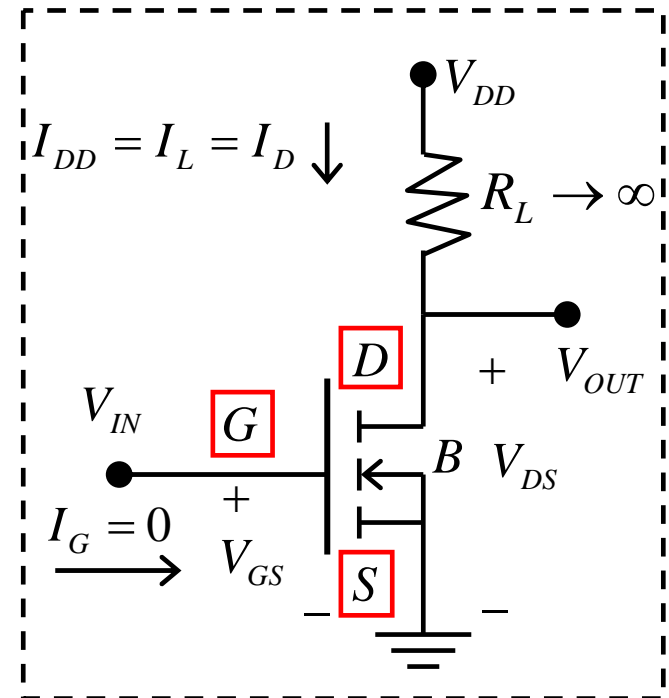Invalid since V_{DS} has to be less than $(V_{GS} - V_{TN})$



Operation of N-MOS with Zero Drain Current

Conclusion :

The use of N-MOS as an output pull-down device is important, i.e. with proper selection of a load device, high V_{GS} results in low V_{DS} .

Resistance of Drain-to-Source (R_{DS})
Channel of NMOS Operating in Linear
Mode (example):



Let : $V_{GS} = 5V$, $V_{TN} = 1V$, $K_n = 40\mu A/V^2$.

Determine R_{DS}

Sol:

$$R_{DS} = \frac{1}{K_n [(V_{GS} - V_{TN}) - V_{DS}]}$$

  It can be seen that the N-MOS operating in linear mode becomes more conductive as V_{DS} decreases.






VTC of N-MOS Loaded with Resistor

Graphical determination of VTC :

$$V_{IN} = V_{GS} \quad , \quad V_{OUT} = V_{DS}$$

$$\text{Load line: } I_L = I_D = \frac{V_{DD} - V_{DS}}{R_L}$$

   From the intersections between the load line and the family of the current-voltage characteristics, the pairs of (V_{IN}, V_{OUT}) can be determined



VTC of N-MOS Loaded with Resistor

Analytical determination of VTC :

V_{OH}

When V_{IN} is low, i.e. $V_{IN} = V_{GS} < V_{TN}$: \rightarrow N_O is cut-off

$$I_L = I_D = 0$$

$$V_{OH} = V_{DD}$$


V_{OL}

For the low output state, the N-MOS operates in linear mode:

$$I_D = \frac{K_n}{2} [2 \times (V_{GS} - V_{TN}) V_{DS} - V_{DS}^2]$$

Now, just as an assumption that the MOS is driven by a similar gate, i.e. $V_{IN} = V_{OH} = V_{DD}$.
 
$$I_D = \frac{K_n}{2} [2 \times (V_{DD} - V_{TN}) V_{DS} - V_{DS}^2] = \frac{V_{DD} - V_{DS}}{R_L}$$



VTC of N-MOS Loaded with Resistor

Analytical determination of VTC :

V_{OL}


$$V_{OL}^2 - 2 \left[V_{DD} - V_{TN} + \frac{1}{K_n R_L} \right] V_{OL} + \frac{2}{K_n} \frac{V_{DD}}{R_L} = 0 \quad (*)$$

$$V_{OL} = \left[V_{DD} - V_{TN} + \frac{1}{K_n R_L} \right] \pm \sqrt{\left[V_{DD} - V_{TN} + \frac{1}{K_n R_L} \right]^2 - \frac{2}{K_n} \frac{V_{DD}}{R_L}}$$

OR: neglecting V_{OL}^2 in (*)

$$V_{OL} = \frac{V_{DD}}{K_n R_L \left[\frac{K_n R_L}{(V_{DD} - V_{TN}) K_n R_L + 1} \right]}$$
 
$$V_{OL} = \frac{V_{DD}}{(V_{DD} - V_{TN}) K_n R_L + 1} = V_{DS} \leq (V_{GS} - V_{TN})$$



To ensure that N_O operates in linear mode

VTC of N-MOS Loaded with Resistor

Analytical determination of VTC :

V_{IL}

V_{IL} in MOSFET is defined as the input voltage slightly below $V_{OUT} = V_{OH}$ where $\text{slope} = -1$ or

$$\frac{dV_{OUT}}{dV_{IN}} = -1$$


For low input voltages (i.e. $V_{OUT} \rightarrow V_{OH}$), N_o is in saturation

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 \Rightarrow I_D = \frac{K_n}{2} (V_{IN} - V_{TN})^2$$

$$\& \quad I_D = \frac{V_{DD} - V_{DS}}{R_L} \Rightarrow I_D = \frac{V_{DD} - V_{OUT}}{R_L}$$

$$\frac{dV_{OUT}}{dV_{IN}} = \frac{d}{dV_{IN}} \left(V_{DD} - \frac{R_L K_n}{2} (V_{IN} - V_{TN})^2 \right) = -1 \Rightarrow -R_L K_n (V_{IN} - V_{TN}) = -1$$
 
$$V_{IN} = V_{IL} = \frac{1}{R_L K_n} + V_{TN}$$




VTC of N-MOS Loaded with Resistor

Analytical determination of VTC :

V_{IH} in MOSFET is defined as the input voltage slightly before $V_{OUT} = V_{OL}$ where **slope = -1** or $\frac{dV_{OUT}}{dV_{IN}} = -1$

 For high input voltages (i.e. $V_{OUT} \rightarrow V_{OL}$), N_O is in linear operation



$$I_D = \frac{K_n}{2} [2 \times (V_{GS} - V_{TN}) V_{DS} - V_{DS}^2] \Rightarrow I_D = \frac{K_n}{2} [2 \times (V_{IN} - V_{TN}) V_{OUT} - V_{OUT}^2]$$

$$\& \quad I_D = \frac{V_{DD} - V_{DS}}{R_L} \Rightarrow I_D = \frac{V_{DD} - V_{OUT}}{R_L}$$

$$V_{OUT}(IH) = \frac{V_{IH} - V_{TN}}{2} + \frac{1}{2R_L K_n}$$



$$V_{IH} - V_{TN} = \frac{\frac{-1}{2R_L} \pm \sqrt{\left(\frac{1}{2R_L}\right)^2 + \frac{3}{2} \frac{V_{DD}}{R_L} K_n}}{\frac{3}{4} K_n}$$

must $V_{DS} \leq (V_{GS} - V_{TN})$ i.e. $V_{OUT}(IH) \leq (V_{IH} - V_{TN})$

VTC of N-MOS Loaded with Resistor

Analytical determination of VTC :

V_M Mid point

$$V_{OUT} = V_{IN} = V_M$$

$$\Rightarrow V_{DS} = V_{OUT} = V_M \quad \& \quad V_{GS} = V_{IN} = V_M$$

$$\begin{aligned} V_{DS}(sat) &= V_{GS} - V_{TN} \\ &= V_{DS} - V_{TN} \end{aligned}$$


$$\Rightarrow V_{DS}(sat) < V_{DS}$$

N_O is in saturation operation


$$I_D = \frac{K_n}{2} (V_M - V_{TN})^2 \quad \& \quad I_D = \frac{V_{DD} - V_M}{R_L}$$

$$\frac{K_n}{2} (V_M^2 - 2V_M V_{TN} + V_{TN}^2) = \frac{V_{DD}}{R_L} - \frac{V_M}{R_L}$$

Then solve for V_M

 

VTC of N-MOS Loaded with Resistor

 

● Example

Calculate the critical values of the VTC of a resistor loaded NMOS inverter shown previously assuming:


$$V_{DD}=5V, V_T=1V, \underline{k_n=40\mu A/V^2}, R_L=50k\Omega,$$

● Solution

$$V_{OH} = V_{DD} = 5V$$

$$V_{OL} = \frac{V_{DD}}{(V_{DD} - V_{TN})K_n R_L + 1} = \frac{5}{(5-1)40 \times 10^{-3} \times 50 + 1} = 0.5556V$$

 
$$V_{IL} = \frac{1}{R_L K_n} + V_{TN} = \frac{1}{50 \times 40 \times 10^{-3}} + 1 = 1.5V$$



$$0.556 \leq (5-1) \text{ ok!}$$

Slide 8

VTC of N-MOS Loaded with Resistor

 

Example

Calculate the critical values of the VTC of a resistor loaded NMOS inverter shown previously assuming:

$$V_{DD}=5V, V_T=1V, k_n=40\mu A/V^2, R_L=50k\Omega,$$

Solution


$$V_{IH} - V_{TN} = \frac{\frac{-1}{2R_L} \pm \sqrt{\left(\frac{1}{2R_L}\right)^2 + \frac{3}{2} \frac{V_{DD}}{R_L} K_n}}{\frac{3}{4} K_n}$$

$$V_{IH} - V_{TN} = 2.27 \text{ or } -2.94$$

$$V_{IH} = 3.27V$$


$$V_{OUT}(IH) = \frac{V_{IH} - V_{TN}}{2} + \frac{1}{2R_L K_n} = \frac{2.27}{2} + \frac{1}{4} = 1.39V$$

must $V_{DS} \leq (V_{GS} - V_{TN})$ ok!

 

Slide 10

VTC of N-MOS Loaded with Resistor

 

- Example

Calculate the critical values of the VTC of a resistor loaded NMOS inverter shown, assuming:

$$V_{DD}=5V, V_T=1V, k_n=40\mu A/V^2, R_L=50k\Omega,$$

- Solution

Solve for V_M

$$\frac{K_n}{2} (V_M^2 - 2V_M V_{TN} + V_{TN}^2) = \frac{V_{DD}}{R_L} - \frac{V_M}{R_L}$$

$$V_M = 2.56V$$

